

Hand Calculation: Ideal Linear Resistor

Given

Quantity	Symbol	Value
Resistance	R	1 k Ω
Evaluation voltage	V	5 V
LTspice measured current	I_{SPICE}	4.99999988824 mA

Analytical current

For an ideal resistor, Ohm's law gives

$$[I = \frac{V}{R}]$$

Therefore,

$$[I_{\text{analytical}} = \frac{5\,\mathrm{V}}{1000\,\Omega} = 0.005\,\mathrm{A} = 5.000000\,\mathrm{mA}]$$

Conductance

$$[G = \frac{1}{R} = \frac{1}{1000\,\Omega} = 1\,\mathrm{mS}]$$

The slope of the I–V curve is therefore 1 mS .

Power at 5 V

Using the passive-resistor relationship,

$$[P = VI = \frac{V^2}{R}]$$

$$[P_{5V} = \frac{(5\,\mathrm{V})^2}{1000\,\Omega} = 0.025\,\mathrm{W} = 25\,\mathrm{mW}]$$

Analytical versus SPICE comparison

The absolute current error is

$$[\left| I_{\text{SPICE}} - I_{\text{analytical}} \right| = \left| 4.99999988824 - 5.00000000000 \right| \,\mathrm{mA} = 0.00000011176\,\mathrm{mA}]$$

or approximately 0.11176 nA .

The relative error is

$$\left[\epsilon_r = \frac{|I_{\text{SPICE}} - I_{\text{analytical}}|}{I_{\text{analytical}}} \times 100 \approx 2.24 \times 10^{-6} \% \right]$$

This is numerical solver and display precision, not a physical modelling discrepancy. The ideal resistor model is linear and has no tolerance or temperature coefficient in this experiment.

Conclusion

At $V = 5 \text{ V}$, the analytical current is 5 mA and LTspice reports 4.99999988824 mA . The result verifies Ohm's law and the expected 1 mS I–V slope within numerical precision. The corresponding ideal-resistor power is 25 mW .